


硬體描述語言作業一

B023040018 傅正安

Structure-Level modeling

```
1  module half_adder(S,C,x,y);
2      output S,C;
3      input x,y;
4      xor(S,x,y);
5      and(C,x,y);
6  endmodule
7
8  module full_adder(S,C,x,y,z);
9      output S,C;
10     input x,y,z;
11     wire S1,C1,C2;
12     half_adder HA1 (S1,C1,x,y);
13     half_adder HA2 (S,C2,S1,z);
14     or(C,C2,C1);
15 endmodule
16
17 module adder_struct(sum,cout,a,b,cin);
18     output [7:0] sum;
19     output cout;
20     input [7:0] a,b;
21     input cin;
22     wire C1,C2,C3,C4,C5,C6,C7;
23     full_adder FA0(sum[0],C1,a[0],b[0],cin),
24     FA1(sum[1],C2,a[1],b[1],C1),
25     FA2(sum[2],C3,a[2],b[2],C2),
26     FA3(sum[3],C4,a[3],b[3],C3),
27     FA4(sum[4],C5,a[4],b[4],C4),
28     FA5(sum[5],C6,a[5],b[5],C5),
29     FA6(sum[6],C7,a[6],b[6],C6),
30     FA7(sum[7],cout,a[7],b[7],C7);
31 endmodule
32
```



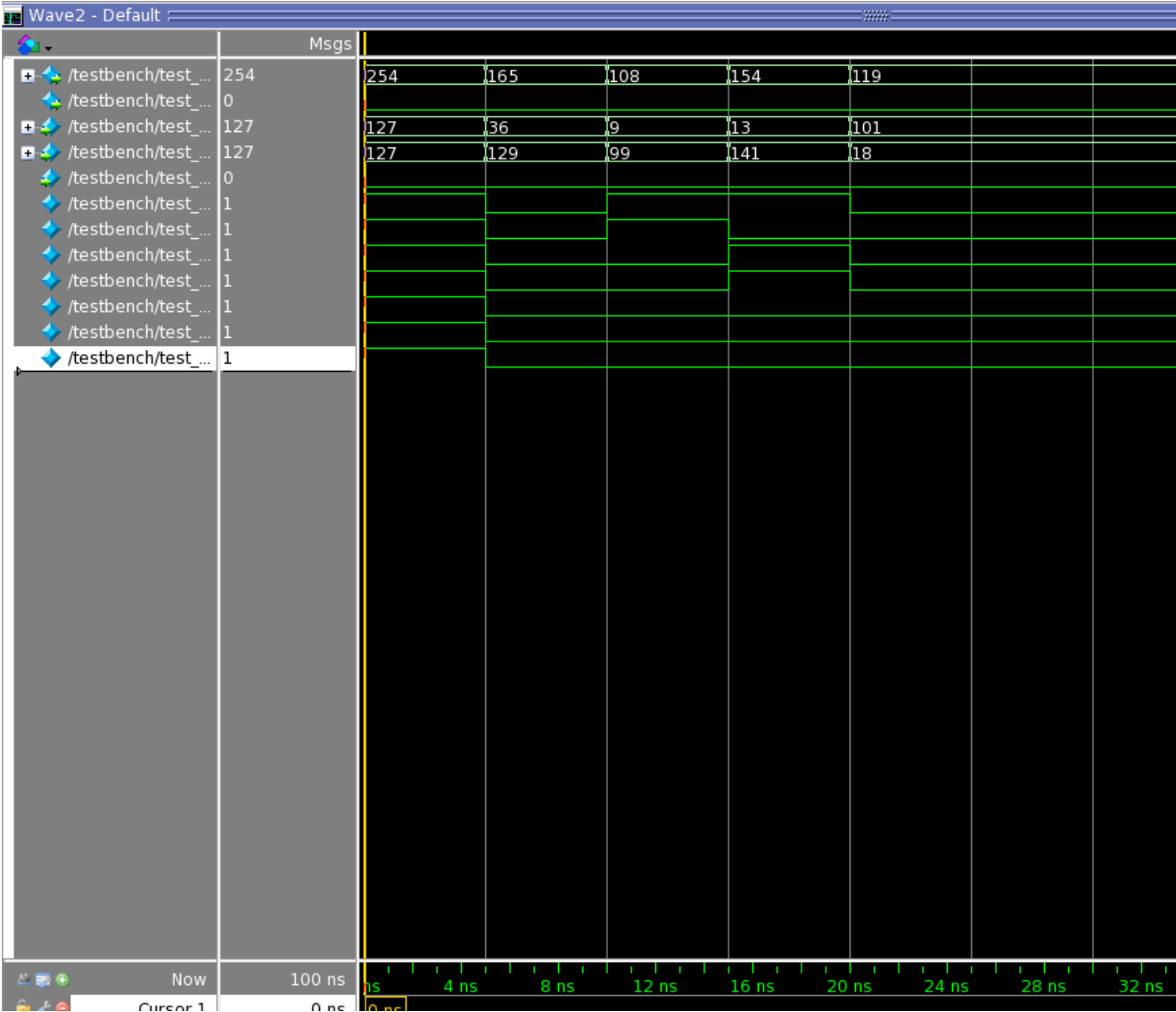









產生的波形圖



加上 D-Flip-Flop

```
1  module adder_struct_dff(sum,carry,a,b,cin,clock);
2      output [7:0]sum;
3      output carry;
4      input [7:0] a;
5      input [7:0] b;
6      input cin;
7      input clock;
8      wire [7:0] sum_temp;
9      wire carry_temp;
10     adder_struct adder(sum_temp,carry_temp,a,b,cin);
11     D_FF dff0(sum[0],sum_temp[0],clock),
12         dff1(sum[1],sum_temp[1],clock),
13         dff2(sum[2],sum_temp[2],clock),
14         dff3(sum[3],sum_temp[3],clock),
15         dff4(sum[4],sum_temp[4],clock),
16         dff5(sum[5],sum_temp[5],clock),
17         dff6(sum[6],sum_temp[6],clock),
18         dff7(sum[7],sum_temp[7],clock),
19         dff8(carry,carry_temp,clock);
20 endmodule
21
```

把結果先存到 flip flop 裡面，等到 clock 為正時產生結果

  /testbench_dff/test_struct_dff/sum	119					
 /testbench_dff/test_struct_dff/carry	0					
  /testbench_dff/test_struct_dff/a	101	127	36	9	13	101
  /testbench_dff/test_struct_dff/b	18	127	129	99	141	18
 /testbench_dff/test_struct_dff/cin	0					
 /testbench_dff/test_struct_dff/clock	0					
  /testbench_dff/test_struct_dff/sum_temp	119	254	165	108	154	119
 /testbench_dff/test_struct_dff/carry_temp	0					

Data flow

```
1  module adder_dataflow (sum, carry, a, b, cin);
2      input [7:0] a, b;
3      input cin;
4      output [7:0] sum;
5      output carry;
6      assign {carry, sum} = a + b + cin;
7  endmodule
8
9
```


Wave1 - Default		Msgs							
/testbench/test_...		101	127	36	9	13	101		
[7]		0							
[6]		1							
[5]		1							
[4]		0							
[3]		0							
[2]		1							
[1]		0							
[0]		1							
/testbench/test_...		18	127	129	99	141	18		
[7]		0							
[6]		0							
[5]		0							
[4]		1							
[3]		0							
[2]		0							
[1]		1							
[0]		0							
/testbench/test_...		0							
/testbench/test_...		119	254	165	108	154	119		
[7]		0							
[6]		1							
[5]		1							
[4]		1							
[3]		0							
[2]		1							
[1]		1							
[0]		1							
/testbench/test_...		0							

配上 DFF

```


1  module adder_dataflow_dff(sum,carry,a,b,cin,clock);
2      output [7:0]sum;
3      output carry;
4      input [7:0] a;
5      input [7:0] b;
6      input cin;
7      input clock;
8      wire [7:0] sum_temp;
9      wire carry_temp;
10     adder_dataflow adder(sum_temp,carry_temp,a,b,cin);
11     D_FF dff0(sum[0],sum_temp[0],clock),
12         dff1(sum[1],sum_temp[1],clock),
13         dff2(sum[2],sum_temp[2],clock),
14         dff3(sum[3],sum_temp[3],clock),
15         dff4(sum[4],sum_temp[4],clock),
16         dff5(sum[5],sum_temp[5],clock),
17         dff6(sum[6],sum_temp[6],clock),
18         dff7(sum[7],sum_temp[7],clock),
19         dff8(carry,carry_temp,clock);
20 endmodule
21
22

```

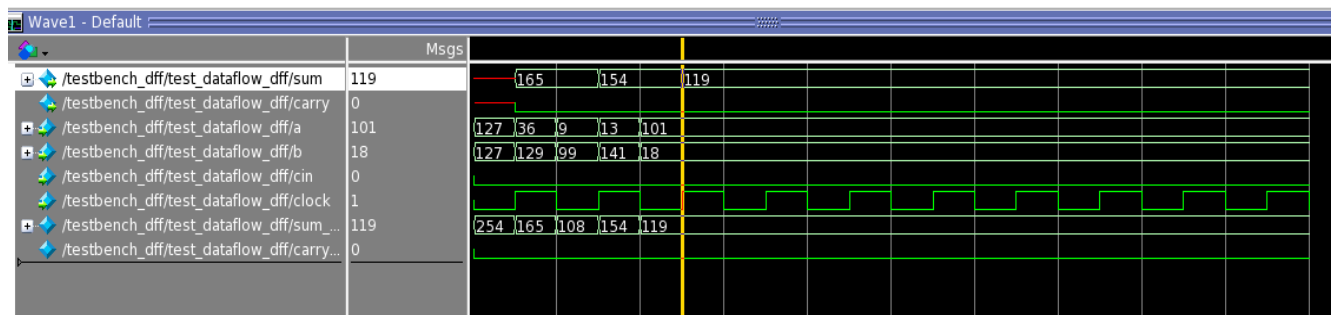

Behavioral modeling
 
```
1  module adder_beh(sum, carry, a, b, cin);
2      input [7:0] a, b;
3      input cin;
4      output [7:0] sum; reg [7:0] sum;
5      output carry; reg carry;
6      always @(a, b, cin)
7      begin
8          {carry, sum} = a + b + cin;
9      end
10 endmodule
```



附上 Testbench

```
h /home/B023040018/8bitadder_test.v (/testben
Ln#
1  module testbench;
2
3      reg [7:0] a;
4      reg [7:0] b;
5      reg cin;
6
7      wire [7:0] behave_sum;
8      wire [7:0] dataflow_sum;
9      wire [7:0] struct_sum;
10     wire behave_carry;
11     wire dataflow_carry;
12     wire struct_carry;
13
14     adder_beh test_behave (
15         .sum(behave_sum),
16         .carry(behave_carry),
17         .a(a),
18         .b(b),
19         .cin(cin)
20     );
21     adder_dataflow test_dataflow(
22         .sum(dataflow_sum),
23         .carry(dataflow_carry),
24         .a(a),
25         .b(b),
26         .cin(cin)
27     );
28
29     adder_struct test_struct(
30         .sum(struct_sum),
31         .cout(struct_carry),
32         .a(a),
33         .b(b),
34         .cin(cin)
35     );
36
37
38     initial begin
39         a = 8'b01111111;
40         b = 8'b01111111;
41         cin = 0;
42         #5
43         a = $random;
44         b = $random;
45         cin = 0;
46         #5
47         a = $random;
48         b = $random;
49         cin = 0;
50         #5
51         a = $random;
```


DFF 的 testbench

```
1  module testbench_dff;
2
3      reg [7:0] a;
4      reg [7:0] b;
5      reg cin;
6      reg clock;
7
8      wire [7:0] dataflow_sum;
9      wire [7:0] beh_sum;
10     wire [7:0] struct_sum;
11     wire dataflow_carry;
12     wire beh_carry;
13     wire struct_carry;
14     always
15     begin
16         clock = 0; #5;
17         clock = 1; #5;
18     end
19
20     adder_dataflow_dff test_dataflow_dff(
21         .sum(dataflow_sum),
22         .carry(dataflow_carry),
23         .a(a),
24         .b(b),
25         .cin(cin),
26         .clock(clock)
27     );
28     adder_struct_dff test_struct_dff(
29         .sum(struct_sum),
30         .carry(struct_carry),
31         .a(a),
32         .b(b),
33         .cin(cin),
34         .clock(clock)
35     );
36     adder_beh_dff test_beh_dff(
37         .sum(beh_sum),
38         .carry(beh_carry),
39         .a(a),
40         .b(b),
41         .cin(cin),
42         .clock(clock)
43     );
44
45
46
47     initial begin
48         a = 8'b01111111;
49         b = 8'b01111111;
50         cin = 0;
51         #5
```